

DATED
03/04/2020

ASSIGNMENT - 3
BASICS OF ELECTRONICS & COMM ENGG.


72

Submitted by: YASH VINAYVANSHI
B.TECH (2nd SEM)
SECTION C-72
JAMIA MILIA ISLAMIA FET.

Submitted to: PROF. ZEENAT SHAREEF
DEPT. OF ECE
JMIFET.

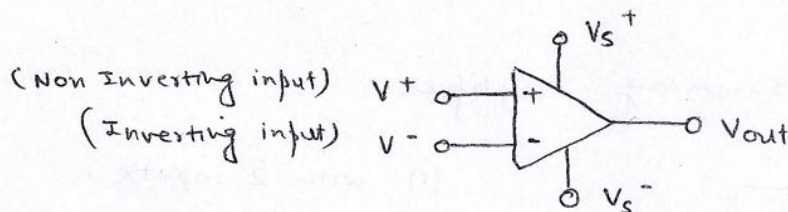Q1. (i) Operational Amplifier

It is a DC coupled, high gain electronic voltage amplifier with two differential inputs and a single ended output. It usually uses feedback to control its overall response characteristics.



(ii) Characteristics of Practical op Amp

Ideal opamp characteristics

- infinite gain
- infinite input impedance
- zero output resistance
- infinite bandwidth
- No offset i.e. $V_{out} = 0$ when $V_{in} = 0$
- Common mode rejection ratio = ∞
- ∞ slew rate




practically
($\sim 10^5$ to 10^6)
($\sim 10^{12}$)
($\sim 10^3$ of Ω)
(limited by slew rate $\neq \infty$)
($\sim mV/s$)
($\sim 10^5$ of dB) $\sim 10^5$ dB
($\sim 10^6$ / sec)

A practical opamp exhibits imperfections from ideal characteristics due to practical limitations as:

- improper matching of transistors in differential stage
- bulk and parasitic capacitance
- ∴ so on.

Voltage transfer characteristics of practical opamp


The maximum output of an opamp is limited by DC supply voltages supplied to opamp. At most, output voltage excursions are limited within V_{s+} , V_{s-} where V_s is power supply voltage. Similarly output currents from the opamp are also limited by these saturation voltages. Between sat voltages, op-amp works as a linear voltage amplifier with slope given as $\frac{V_{output}}{V_{input}}$ representing open loop gain (i.e. when no feedback is used)

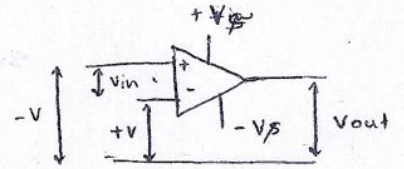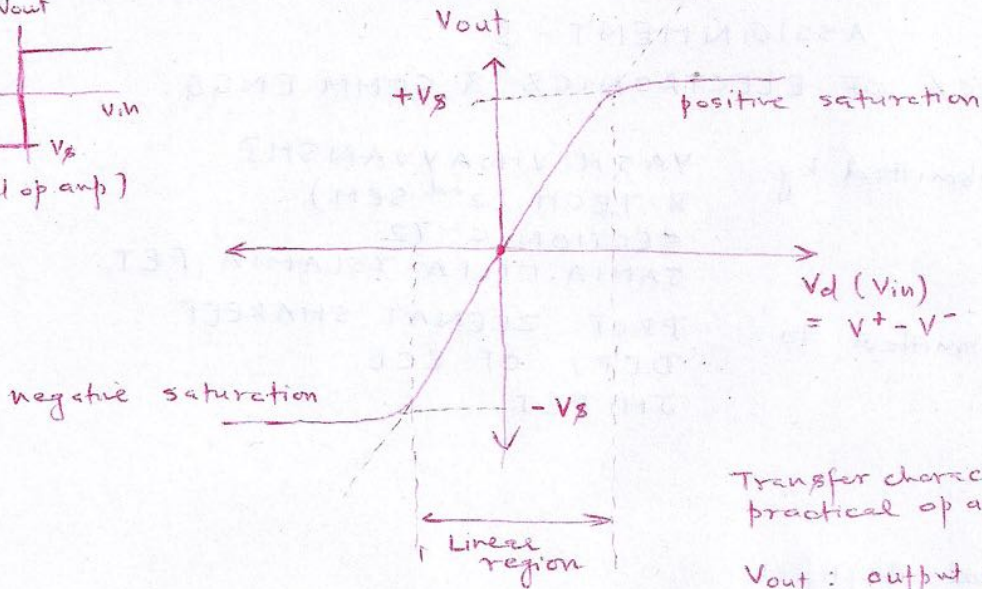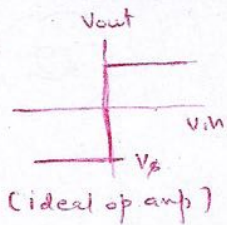

Transfer characteristics of practical op amp.

- V_{out} : output voltage.
- V_d : differential voltage.
- V^+ : non inverting input.
- V^- : inverting input.
- V_s : DC source voltage / saturation voltage.

Q2. Non inverting Summing Amplifier.

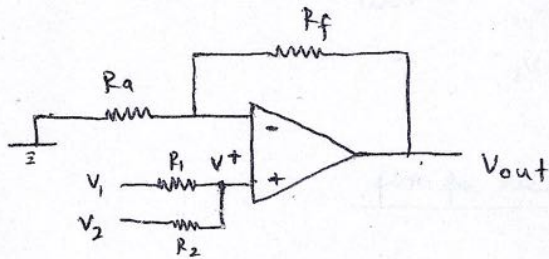

(i) with 2 inputs.

$$V_{out} = \left(1 + \frac{R_f}{R_a}\right) V^+$$

[relⁿ b/w V_{out} & V_{in} for non inverting Amplifier. However due to virtual short $V^+ = V_{in}$]

Applying superposition principle to calculate V^+

effect of V_1

$$V_1^+ = \frac{R_2}{R_1 + R_2} V_1$$

effect of V_2


$$V_2^+ = \frac{R_1}{R_1 + R_2} V_2$$

$$V^+ = V_1^+ + V_2^+ = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

$$\therefore V_{out} = \left(1 + \frac{R_f}{R_a}\right) V^+ = \left(1 + \frac{R_f}{R_a}\right) \left[\frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2 \right]$$

if $R_1 = R_2 = R$ & $R_f = R_a$
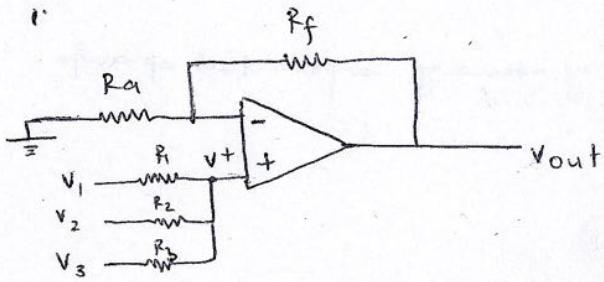
$$V_{out} = (1+1) \left[\frac{V_1 + V_2}{2} \right] = \boxed{V_1 + V_2}$$



(ii) If 3 inputs.


(if $R_1 = R_2 = R_3 = R$)

$$V_1^+ = \frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)} \times V_1 = \frac{V_1}{3}$$

$$V_2^+ = \frac{R_1 \parallel R_3}{R_2 + (R_1 \parallel R_3)} \times V_2 = \frac{V_2}{3}$$

$$V_3^+ = \frac{R_2 \parallel R_1}{R_3 + (R_2 \parallel R_1)} \times V_3 = \frac{V_3}{3}$$
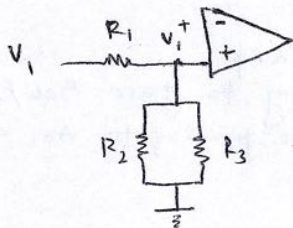
$$V^+ = V_1^+ + V_2^+ + V_3^+ \\ = \frac{V_1 + V_2 + V_3}{3}$$




For neg. feed back (ie Non inverting Amp)

$$V_{out} = \left(1 + \frac{R_f}{R_a}\right) V^+ = \left(1 + \frac{R_f}{R_a}\right) \left(\frac{V_1 + V_2 + V_3}{3}\right)$$

if $1 + \frac{R_f}{R_a} = 3 \sim V_{out} = V_1 + V_2 + V_3$

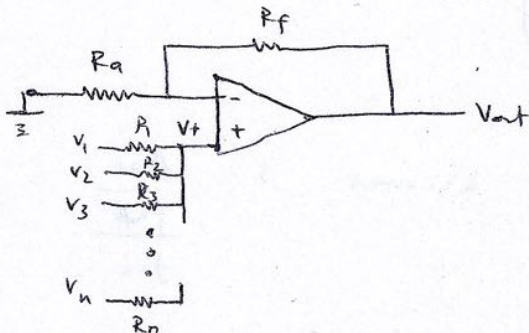(iii) Similar to (i) & (ii). If there are n inputs to be added,




$$V_{out} = V_1 + V_2 + \dots + V_n \\ \text{if } R_1 = R_2 = R_3 = \dots = R_n \\ \& \quad 1 + \frac{R_f}{R_a} = n$$

Limitations of non inverting summing amplifier.

(i) Theoretically, any no. of inputs can be added but practically no. of inputs are limited by V_s ie $V_1 + V_2 + \dots + V_n \leq V_s$

(ii) All individual input voltage sources are not isolated from each other.

Q3

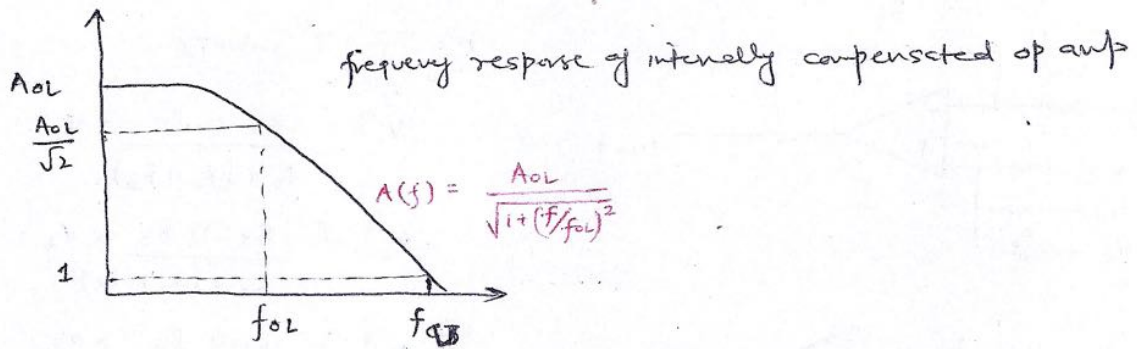

A_{OL} : Maximum open loop gain of op amp.
 (3dB drop frequency) f_{OL} : cutoff freq : freq. corresponding to gain $A_{OL}/\sqrt{2}$.
 f_{u} : bandwidth (unity gain) freq : frequency corresponding to $A_{OL} = 1$

$$|A| = \frac{A_{OL}}{\sqrt{1 + (f/f_{OL})^2}}$$

At $A = 1$, $f = f_u$

$$1 = \frac{A_{OL}}{\sqrt{1 + \left(\frac{f_u}{f_{OL}}\right)^2}}$$


since $f_{OL} \ll f_u$

$$\therefore 1 = \frac{A_{OL}}{\sqrt{\frac{(f_{OL})^2 + (f_u)^2}{(f_{OL})^2}}} \quad \text{becomes} \quad 1 = \frac{A_{OL}}{\frac{f_u}{f_{OL}}}$$

$$\therefore \boxed{f_u = A_{OL} f_{OL}} \quad \text{formula}$$

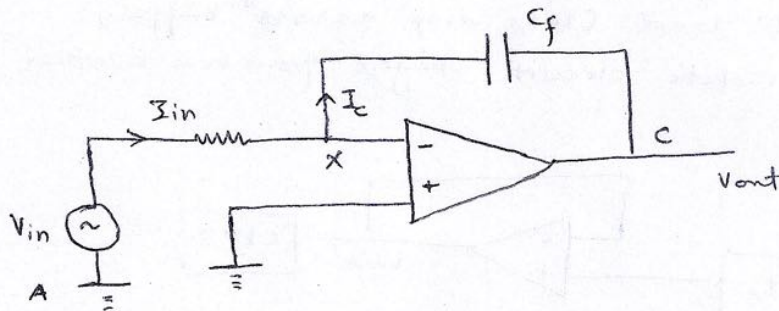Q4. op-amp as an integrator.

If we use a reactive component such as capacitor with an op-amp, we can use it as integrator or differentiator.



Due to virtual short, $V_x = 0$


By KCL from A to C,

$$I_{in} = I_c \quad (0 - V_{out})$$

$$\frac{V_{in} - 0}{R} = C_f \frac{dV_c}{dt}$$

$$\frac{V_{in}}{R} = -C_f \frac{d}{dt} V_{out}$$
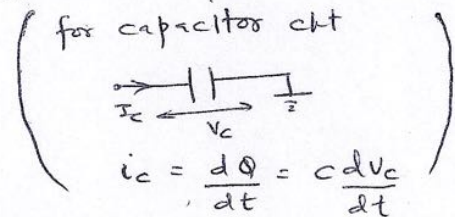
$$\frac{dV_{out}}{dt} = \frac{-1}{RC_f} \times V_{in}(t)$$




$$V_{out}(t) = \frac{-1}{RC_f} \int V_{in}(t) dt + V_{out}(0^+)$$

V_{out} before integration as const of integrator

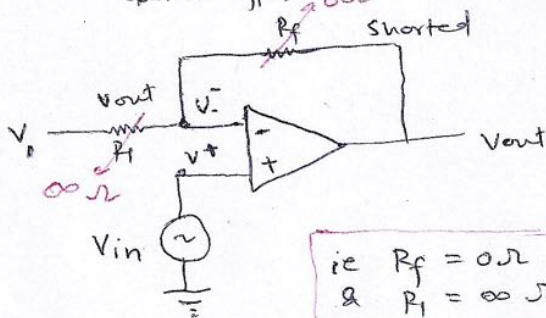Q5. (i) voltage follower / Buffer

A buffer Amplifier is a ckt that provides electrical impedance transformation from one circuit to another with aim of preventing the signal source from being affected by currents or voltages that load is produced with.



$$\text{ie } R_f = 0 \Omega \text{ \& } R_1 = \infty \Omega$$

Due to virtual short b/w inverting & non inverting terminals


$$V^- = V^+$$

$$V^- = V_{in} = V_{out}$$

\therefore output voltage mirrors / follows input voltage.

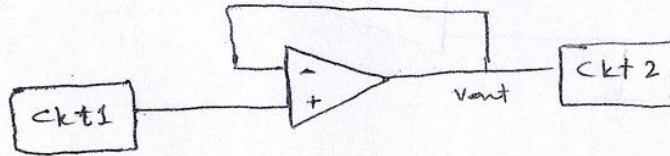(ii) Applications of voltage follower.

- used to provide high input impedance and therefore preventing loading of source.
- low input impedance, maximum of source voltage applied to load (less drop across buffer)
- used to isolate circuit stages from one another.



useful if ckt 2 has low input impedance and can load ckt 1.

— x —